

FPGA Basics 1

Combinational Logic Design in Verilog HDL

What is FPGA?


- ▶ A field-programmable gate array (**FPGA**) is an integrated circuits designed to be configured by a user.
- ▶ The FPGA configuration is generally specified using hardware description language (**HDL**)
- ▶ FPGAs contain an array of programmable logic block and a hierarchy of reconfigurable interconnects that allow the blocks to be wired together.



What can FPGAs be used for?

- ▶ FPGAs can be used to solve any problems which is computable.
- ▶ Hardware acceleration is a main FPGA use case.
- ▶ The advantage lies in that FPGAs are sometimes significantly faster for some application because of their parallel nature.
- ▶ Specific applications of FPGAs include digital signal processing, computer vision, speech recognition, cryptography and a growing range of other areas.

GNSS Receiver Architecture

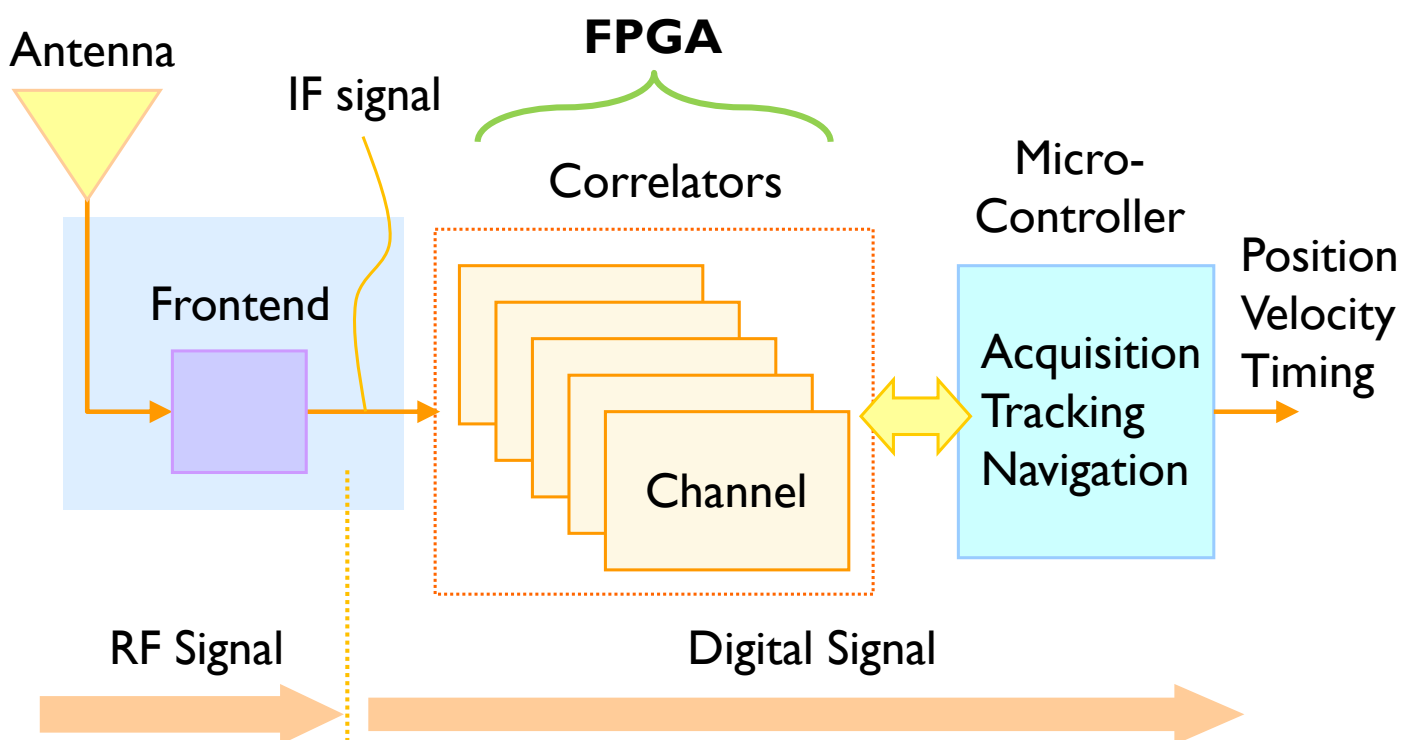


Types of Logic Circuits

- ▶ There are two types of logic circuits depends on their output and memory used.
 - ▶ Combinational logic circuits
 - ▶ Sequential logic circuits
 - ▶ The outputs of a combinational logic circuit are determined from only the present combination of inputs.
 - ▶ The outputs of a sequential logic circuit are determined from both the present combination of inputs and previous outputs. That means sequential logic circuits use memory elements to store the value of previous outputs.
-




Combinational Logic Circuits

 - ▶ Combinational logic circuits are made up from basic logic NAND, NOR or NOT gates that are “combined” together to produce more complicated logic circuits.



Sequential Logic Circuits

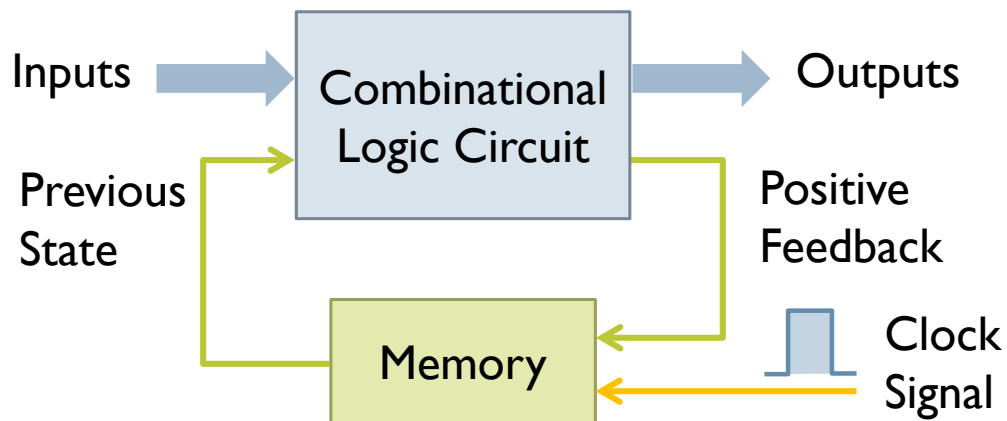- ▶ In sequential logic circuits, the things happen in a “sequence”, one after another, and the clock signal determines when things will happen next.



What is an HDL?


- ▶ Hardware description languages allow you to describe a logic circuit using words and symbols, and then development software can convert that textual description into configuration data that is loaded into the FPGA.
 - ▶ The most popular hardware description languages are Verilog and VHDL.
-

Programming Languages vs. HDLs

- ▶ HDLs resemble high-level programming languages such as C and Python, but it is important to understand that there is a fundamental difference: statements in HDL code involve parallel operation.
 - ▶ When we write a computer program, we understand that the processor will execute lines of code one at a time, following the top-to-bottom organization.
 - ▶ In HDL code, we are describing digital hardware, and separate portion of this hardware can operate simultaneously, even though the corresponding lines of code are written using a top-to-bottom organization.
-

GNSS Correlator Architecture

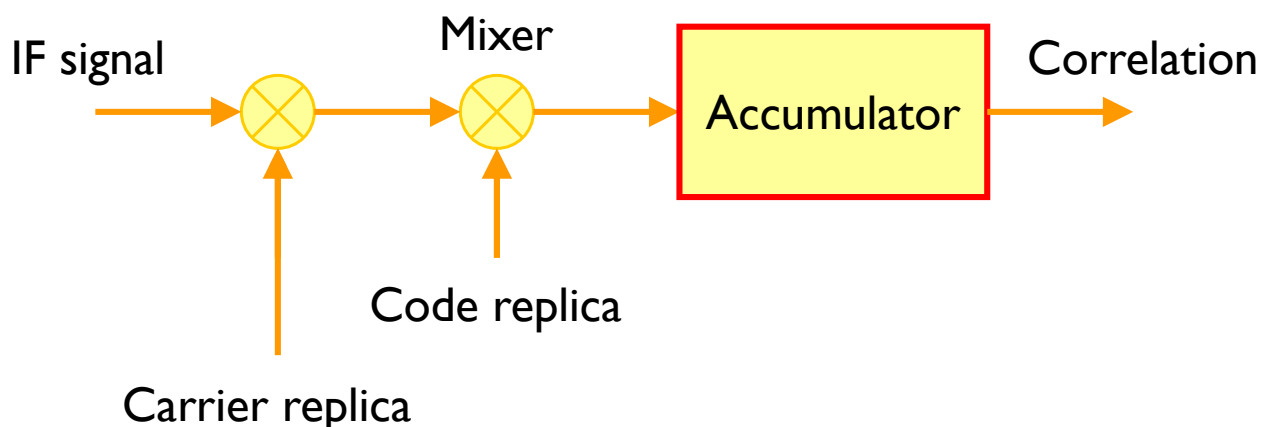- ▶ Correlators are the key operation for GNSS receivers to synchronize with the incoming signal.
- ▶ The maximum correlation peak is acquired when the both code and carrier replicas match the incoming signal.




Binary Addition of Two Bits

- ▶ When the two single bits are added together, the addition of “0+0”, “0+1” and “1+0” results in either a “0” or a “1”.
- ▶ The sum of “1+1” is equal to “2”, but it does not exist in binary.
- ▶ The decimal “2” is equal to the binary “10”, in other words a zero for the sum plus an extra carry bit.

$$\begin{array}{cccc} 0 & 0 & 1 & 1 \\ + 0 & + 1 & + 0 & + 1 \\ \hline 0 & 1 & 1 & 1\ 0 \\ & & & \underbrace{\hspace{1em}}_{\text{Carry}} \underbrace{\hspace{1em}}_{\text{Sum}} \end{array}$$

Half Adder

 

Truth Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\left\{ \begin{array}{l} S = A \text{ XOR } B = A \wedge B \\ C = A \text{ AND } B = A \& B \end{array} \right.$$

Half Adder Verilog Example

```
module half_adder(A, B, S, C);  
  
    input A, B;  
    output S, C;  
  
    assign S = A ^ B;  
    assign C = A & B;  
  
endmodule
```



Modules

- ▶ A “module” is a basic unit in Verilog code that implement a certain functionality.
- ▶ A module should be enclosed within “module” and “endmodule” keywords.
- ▶ Name of the module should be given right after the “module” keyword, and a list of “ports” should be declared as well.

```
module half_adder(A, B, S, C);  
    Name           Ports  
    ...  
endmodule
```



Types of Ports

▶ **input**

- ▶ Simple input
- ▶ The design module can only receive values from outside.

▶ **output**

- ▶ Simple output
- ▶ The design module can only send values to outside.

▶ **inout**

- ▶ Tri-state bi-directional port
- ▶ The design module can either send or receive values.



Wires and Assignments

- ▶ To make a continuous assignment to an internal signal in the module, the signal must first be declared as a “**wire**”.
 - ▶ Ports are by default considered as signals of type “wire”.
- ▶ Any “wire” can be driven continuously with a value by the “**assign**” statement.

```
input A, B;  
output S, C;  
  
assign S = A ^ B;  
assign C = A & B;
```




Bitwise Operators

- ▶ Each bit is operated.
- ▶ Result is the size of the largest operand, and the smaller operand if left extended with zeros to the size of the bigger operand.

Character	Operation
~	NOT (invert) each bit
&	AND each bit
	OR each bit
^	XOR each bit



Full Addder

 


A	B	Cin	Sum	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1



Hierarchical Design in Verilog

 - ▶ A hierarchical methodology is used to design simple components to construct more complex one.
- ▶ For example, the full adder is basically two half adders connected together.




Full Adder Verilog Example

```
module full_adder(A, B, Cin, Sum, Cout);  
  
    input A, B, Cin;  
    output Sum, Cout;  
    wire S1, C1, C2;  
  
    half_adder HA1(A, B, S1, C1);  
    half_adder HA2(S1, Cin, Sum, C2);  
  
    assign Cout = C1 | C2;  
  
endmodule
```

3-Bit Adder

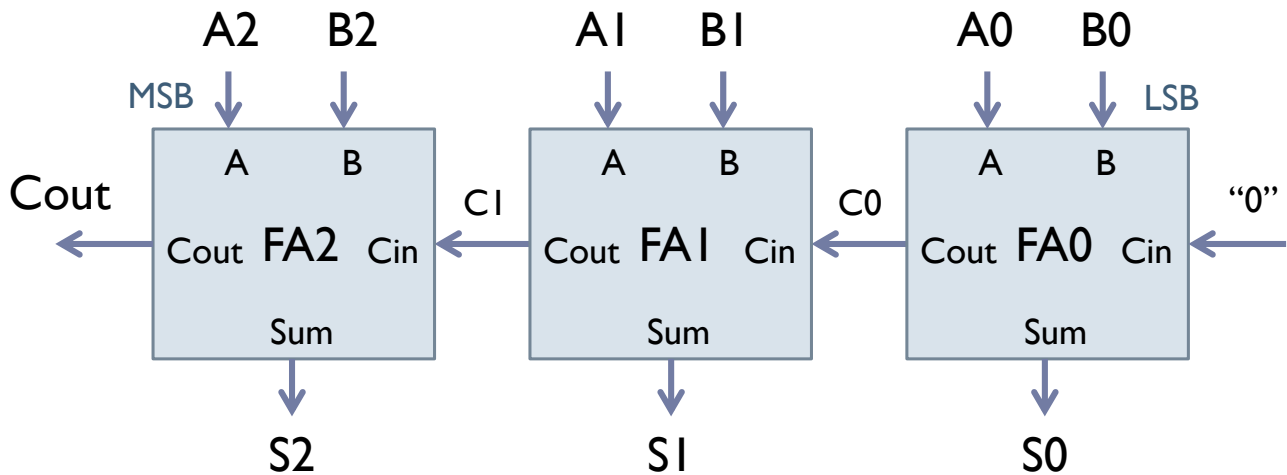- ▶ If you want to N-bit adder, N number of full adders need to be connected or “cascaded” together to produce what is known as a “ripple carry adder”.



3-Bit Adder Verilog Example

```
module adder(A, B, Sum, Cout);  
  
    input [2:0] A, B;  
    output [2:0] Sum;  
    output Cout;  
    wire C0, C1;  
  
    full_adder FA0(A[0], B[0], 0, Sum[0], C0);  
    full_adder FA1(A[1], B[1], C0, Sum[1], C1);  
    full_adder FA2(A[2], B[2], C1, Sum[2], Cout);  
  
endmodule
```

Another 3-Bit Adder Verilog Example

```
module adder3(A, B, Sum, Cout);  
  
    input [2:0] A, B;  
    output [2:0] Sum;  
    output Cout;  
  
    assign {Cout, Sum} = A + B;  
  
endmodule
```



Concatenation Operators


- ▶ Multi-bit wires and variables can be clubbed together using concatenation operators `{` and `}` separated by commas.

```
wire [7:0] high1, low1;  
wire [7:0] high2, low2;  
wire [15:0] data;  
  
assign data = {high1, low1};  
assign {high2, low2} = data;
```



Design Flows

Architecture Design

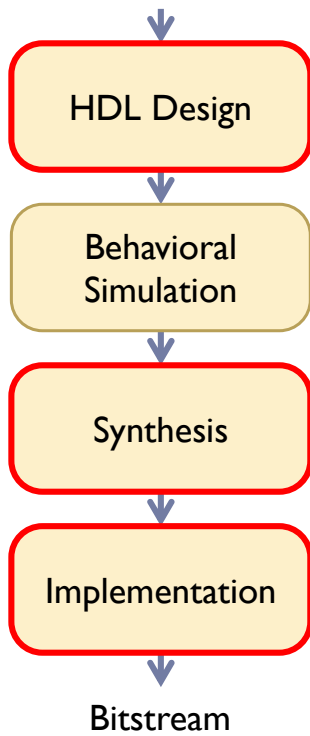

This is the process of creating the hardware logic itself, typically by writing register-transfer level (**RTL**) using a hardware description language (HDL).

This step ensure that the design works as intended using a specified testbench module.

This process transforms the HDL design into a gate level representation (**netlist**).

This step provides all the features necessary to optimize, place and route the netlist onto the available device resources of the target part.

Bitstream
